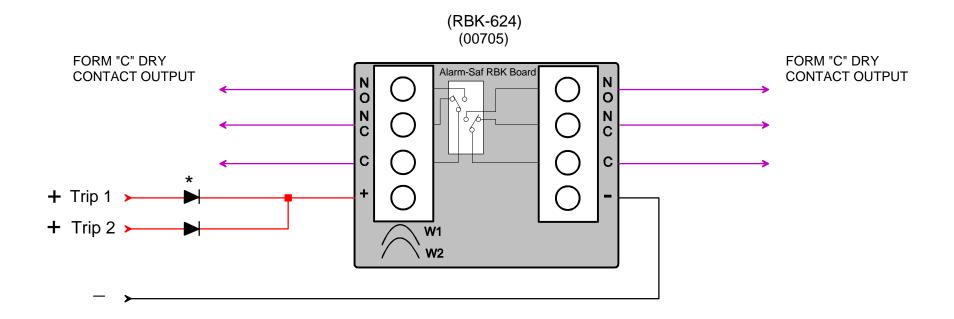


## **Two Input "OR" Function**



Application: For use when two seperate positive trip signals are needed to activate a relay. The relay will activate by applying one or two positive trip signals to the + terminal of the RBK-624.

## Required

<sup>\*</sup> General Purpose Diode (1N4001) to provide isolation between Trip signals.